

EXPERIMENT NO


AIM: To find the polarity and turns ratio of a single phase transformer.

APPARATUS: One transformer, two voltmeters, one autotransformer

THEORY:

It is essential to know the relative polarity at any instant of primary and secondary terminals for making correct connections. When the two transformers are to be connected in parallel to share the load on the system. The marking is correct if voltage E_3 ($E_1 + E_2$ OR $E_1 - E_2$) is less than E_1 , such a polarity is termed as subtractive polarity. The standard practice is to have subtractive polarity because it reduces the voltage stress between adjacent loads. In case $E_3 > E_1$ the emf induced in primary and secondary have additive relation and transformer is said to have additive polarity.

CIRCUITDIAGRAM:

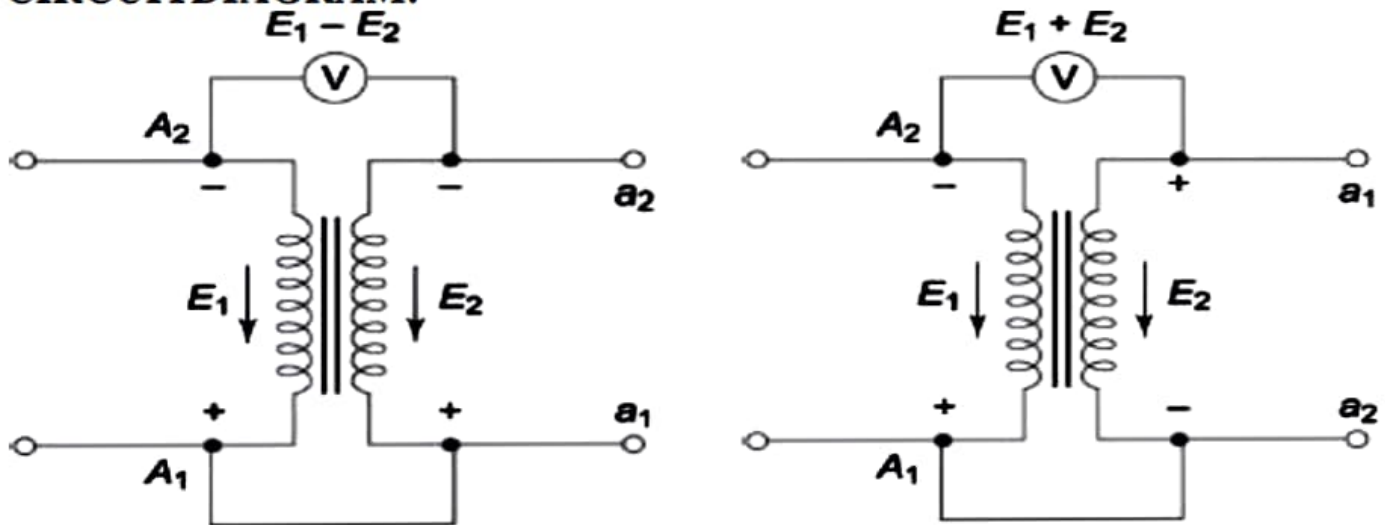

PROCEDURE:

Polarity test:

- connect the circuit as shown in the diagram.
- Switch on the single phase a.c. supply.
- Record the voltages E_1 , E_2 and E_3 . In case $E_3 < E_1$ polarity is subtractive.
- Repeat the step 3 after connecting terminals A_1 and a_2 . In case $E_3 > E_1$ polarity is additive.
- Switch off the a.c. supply

Turn Ratio Test:

- Connect the circuit as shown in the diagram.
- Switch on the a.c. supply.
- Record voltage E_1 across primary and E_2 across various tapping's of secondary.
- If $E_1 > E_2$ then transformer is stepdown.
- If $E_2 > E_1$ then transformer is stepup.
- Switch off a.c. supply

OBSERVATION TABLE:

SUBTRACTIVE-POLARITY:

S.NO.	E_1	E_2	$E_3 = E_2 - E_1$

ADDITIVE-POLARITY:

S.NO.	E_1	E_2	$E_3 = E_1 + E_2$

RESULT:

If $E_2 > E_1$ then transformer is step up otherwise stepdown.